

Design an 8 to 1 MUX using case statement in Verilog HDL

by

Ishraq Ahmed Esha

19301261

A Lab Report 2 submitted to the CSE460 VLSI Design

Course of Sec: 5

Brac University

November 1, 2022

Problem Statement


Design an 8 to 1 MUX using case statement in Verilog HDL

Code


```
module assignment_2(w,s,f);
    input [7:0]w;
    input [2:0]s;
    output reg f;

    always @(w,s)
    begin
        case(s)
            3'b000: f=w[0];
            3'b001: f=w[1];
            3'b010: f=w[2];
            3'b011: f=w[3];
            3'b100: f=w[4];
            3'b101: f=w[5];
            3'b110: f=w[6];
            3'b111: f=w[7];
            default: f=1'b0;
        endcase
    end
endmodule
```


Compilation Report

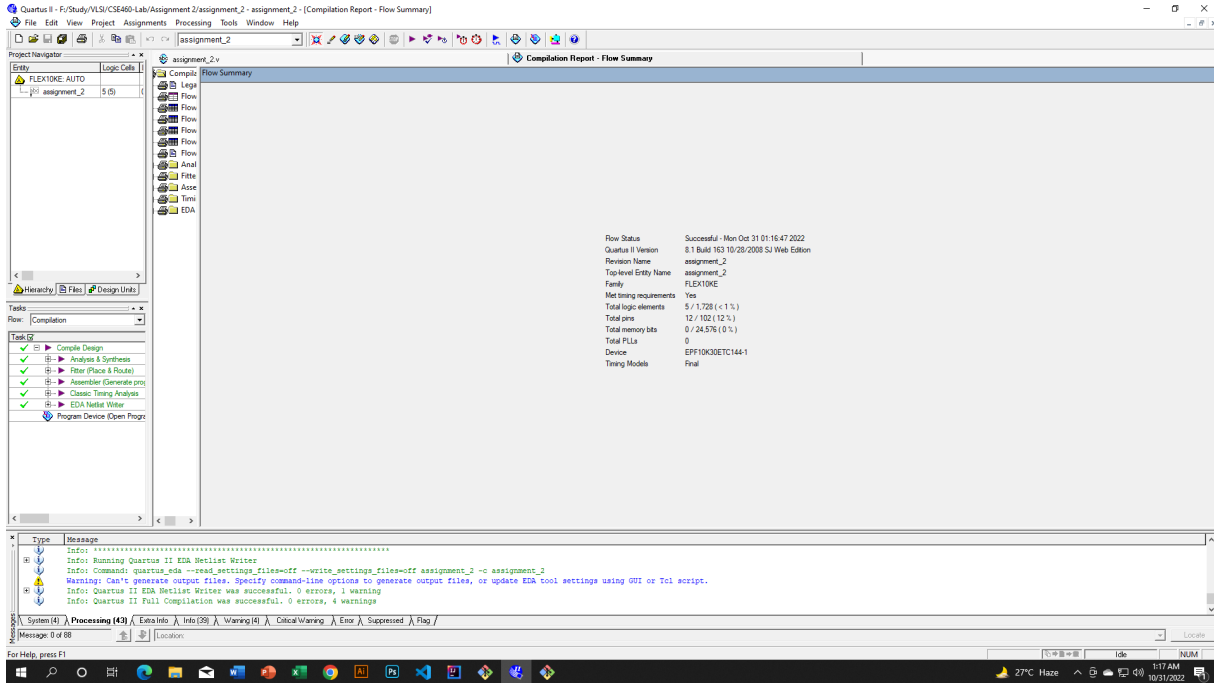

Simulation Report

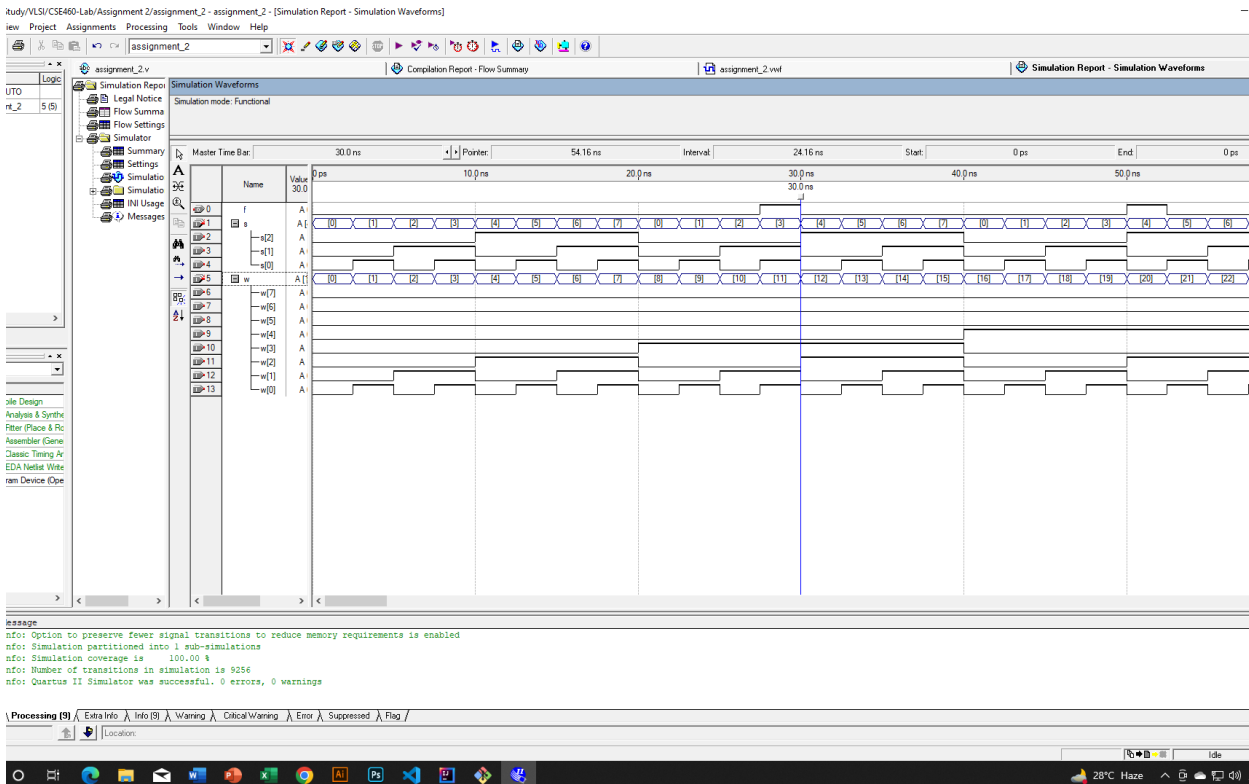

RTL View

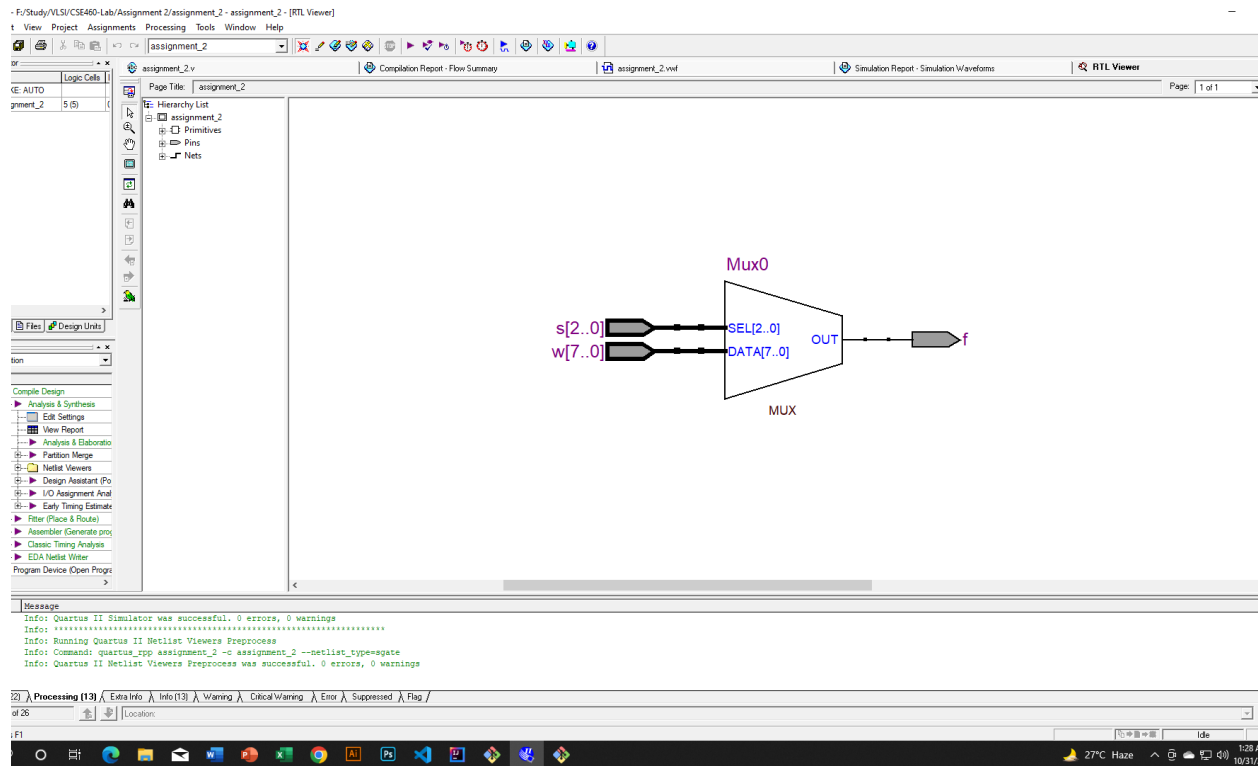

Discussion about the input output from the timing diagram

Here we have 8 input and our system is 8 to 1 MUX. To select the input combination we have 3 pin selection inputs pin which are denoted by s and the main 8 inputs are denoted by w. At the time of 30 ns we get our output high and our chip selection pin is at 0 1 0 . So that means the outpin pin got high at this chip selection combination. There are few other combinations for get the output high.